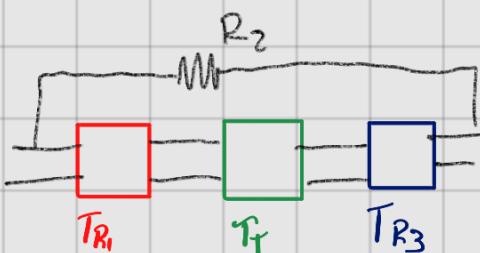


Se pide calcular los parámetros  $Z$

Para facilitar el cálculo separamos en 3 cuadripolos en cascada.




Trafo ideal:

$$T_T = \begin{pmatrix} -a & 0 \\ 0 & -\frac{1}{2} \end{pmatrix}$$

$$T_{R1} = \begin{pmatrix} 1 & 0 \\ \frac{1}{R_1} & 1 \end{pmatrix}$$

$$T_{R2} = \begin{pmatrix} 1 & 0 \\ \frac{1}{R_2} & 0 \end{pmatrix}$$

Nos queda la siguiente cascada

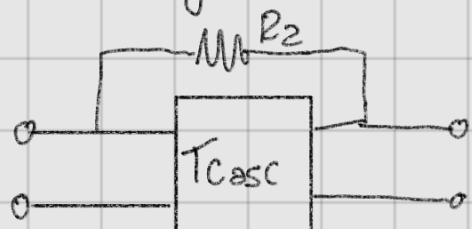

$$T_{\text{casc}} = \begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix} \cdot \begin{pmatrix} -1 & 0 \\ 0 & -1 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ -\frac{1}{3} & -1 \end{pmatrix}$$

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} -1 & 0 \\ -\frac{4}{3} & -1 \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ I_2 \end{pmatrix} \Rightarrow \begin{cases} V_1 = -V_2 \\ I_1 = -\frac{4}{3}V_2 + I_2 \end{cases}$$


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \Rightarrow I_1 = \frac{4}{3}V_1 + I_2 \quad \Rightarrow \quad \frac{V_1}{I_1} = \frac{3}{4} = Z_{11}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \Rightarrow \frac{4}{3}V_2 = I_2 \Rightarrow -\frac{4}{3}V_1 = I_2 \Rightarrow Z_{12} = -\frac{3}{4}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \Rightarrow I_1 = -\frac{4}{3}V_2 + I_2 \quad \Rightarrow \quad Z = -\frac{3}{4}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \Rightarrow Z_{22} = \frac{3}{4}$$

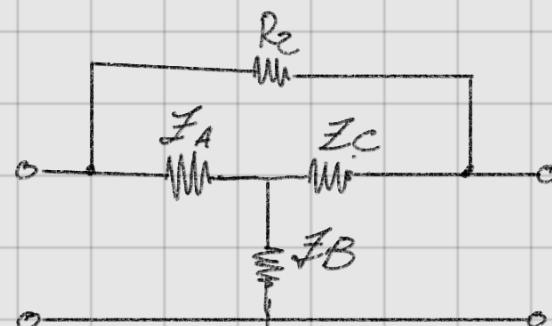
$$Z_{Casc} = \begin{pmatrix} \frac{3}{4} & -\frac{3}{4} \\ -\frac{3}{4} & \frac{3}{4} \end{pmatrix} \Rightarrow$$




$$Z_A = Z_C = Z_{11} - Z_{12} = \frac{6}{4} \leftarrow \text{Por reciprocidad}$$

$$Z_B = Z_{12} = -\frac{3}{4} \quad V_x = 0$$

Circuito Final

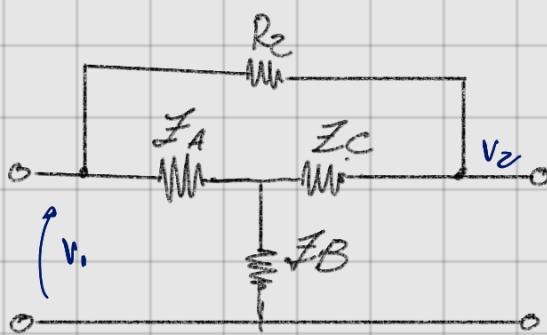


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{3}{10}$$

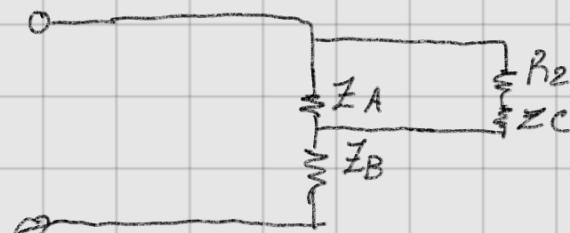

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = -\frac{3}{10}$$

$$\boxed{Z_T \begin{pmatrix} \frac{3}{10} & -\frac{3}{10} \\ -\frac{3}{10} & \frac{3}{10} \end{pmatrix}}$$

## Ejercicio 2

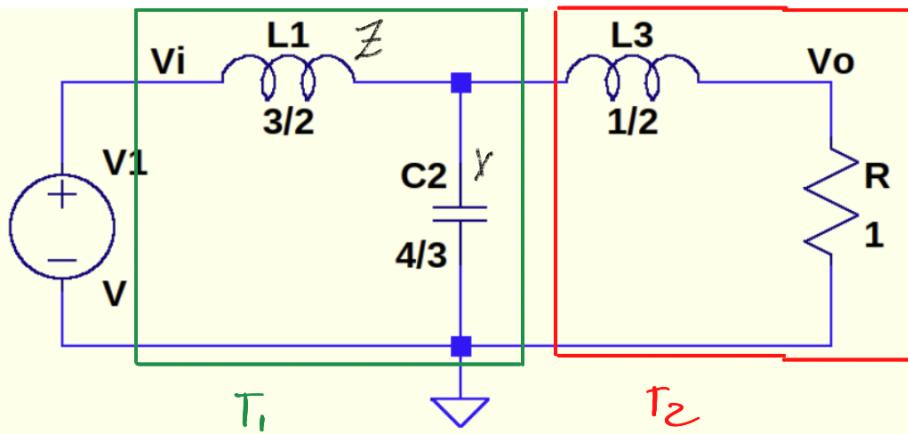

$$T_1 = \begin{pmatrix} 1 + \$L_1 \cdot \$C & \$L_1 \\ \$C & 1 \end{pmatrix}$$

$$T_2 = \begin{pmatrix} 1 + \$L_3 \cdot G & \$L_3 \\ G & 1 \end{pmatrix}$$

$$= \begin{pmatrix} 1 + \$^2 L_1 C & \$L_1 \\ \$C & 1 \end{pmatrix}$$

$$T_2 = \begin{pmatrix} 1 + \$L_3 G & \$L_3 \\ G & 1 \end{pmatrix}$$


$$T_{Casc} = T_1 \cdot T_2 = \begin{pmatrix} \cancel{(1 + \$L_3 G + \$^2 L_1 C + \$^3 L_1 L_3 C G + \$L_1 G)} & \$L_3 + \$^3 L_1 L_3 C + \$C \\ \cancel{\$C + \$^2 L_3 G C + G} & \$^2 C L_3 + 1 \end{pmatrix}$$

$$A = \frac{V_o}{V_i} \Big|_{I_2=0} \Rightarrow \frac{V_o}{V_i} = \frac{1}{A} \Rightarrow$$

$$\frac{R}{L_1 C_2 L_3} \over \frac{\$^3}{L_3} + \$^2 \frac{R}{L_3} + \$ \frac{L_1 + L_3}{L_1 C_2 L_3} + \frac{R}{L_1 C_2 L_3}$$

$$\frac{V_0}{V_i} = \frac{1}{\$^3 + 2\$^2 + 2\$ + 1}$$

## Construcción de MAI

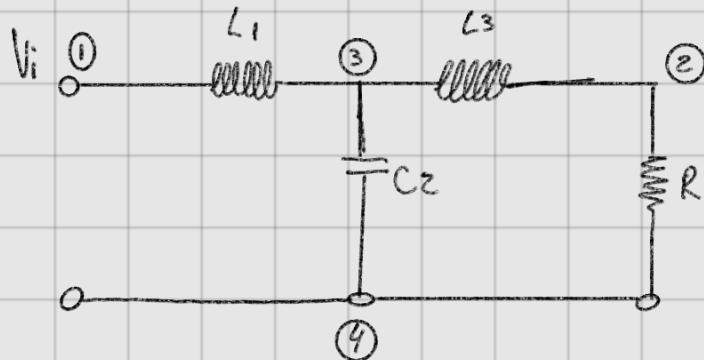

$$MAI = \begin{bmatrix} \frac{1}{\$L_1} & 0 & -\frac{1}{\$L_1} & 0 \\ 0 & \frac{1}{\$L_3} + \frac{1}{R} & -\frac{1}{\$L_3} & -\frac{1}{R} \\ -\frac{1}{\$L_1} & -\frac{1}{\$L_3} & \frac{L_1+L_3 + \$C_2}{\$L_1\$L_3} & -\$C_2 \\ 0 & -\frac{1}{R} & -\$C_2 & \frac{\$C_2 + 1}{R} \end{bmatrix}$$

$$\frac{1}{\$L_1} + \frac{1}{\$L_3} = \frac{1}{\$(L_1+L_3)}$$

## Transferencia usando MAI

$$A_{mn}^{ij} = \frac{V_{ij}}{V_{mn}} = Sg(m-n) \cdot Sg(i-j) \cdot \frac{Y_{ij}}{Y_{mn}}$$

$$V_i = V_{14} \quad V_0 = V_{24}$$

$$Sg(1-4) = -1 = Sg(2-4) \Rightarrow 1 \cdot \frac{Y_{24}}{Y_{14}^{14}}$$

$$Y_{14}^{14} = \begin{vmatrix} \frac{1}{\$L_3} + \frac{1}{R} & -\frac{1}{\$L_3} \\ -\frac{1}{\$L_3} & \frac{L_1+L_3 + \$C_2}{\$L_1\$L_3} \end{vmatrix} = \frac{R + \$L_3}{\$RL_3} \cdot \frac{L_1+L_3}{\$L_1\$L_3} - \frac{1}{\$^2L_3^2}$$

$$\left[ \begin{array}{cccc} \frac{1}{\$L_1} & 0 & -\frac{1}{\$L_2} & 0 \\ 0 & \frac{1}{\$L_3} + \frac{1}{R} & -\frac{1}{\$L_3} & -\frac{1}{R} \\ -\frac{1}{\$L_1} & -\frac{1}{\$L_3} & \frac{1}{\$L_1 + \$L_3} + \$C_2 & -\$C_2 \\ 0 & -\frac{1}{R} & -\$C_2 & \frac{\$C_2 + 1}{R} \end{array} \right] \underline{Y}_{14} = \left[ \begin{array}{c} 0 \\ -\frac{1}{\$L_1} \\ \frac{(\$L_1 + \$L_3)}{\$L_1 L_3 C} + \$C \\ \frac{1}{\$L_1 L_3 C} \end{array} \right] = \frac{1}{\$^2 L_1 L_3}$$

$$\frac{V_0}{V_i} = \frac{\cancel{\frac{1}{\$L_1 L_3 C}}}{\frac{\$L_3^2 + R(L_3 - 1)}{\cancel{\$^2 L_3^2 R}}} = \frac{\frac{R}{L_1 L_3 C}}{\$^3 + \$^2 \frac{R}{L_3} + \frac{\$(L_1 + L_3)}{L_1 L_3 C} + \frac{R}{L_1 L_3 C}}$$

$$\underline{Y}_{14} = \left[ \begin{array}{cc} \frac{1}{\$L_3} + \frac{1}{R} & -\frac{1}{\$L_3} \\ -\frac{1}{\$L_3} & \frac{L_1 + L_3}{\$L_1 + \$L_3} + \$C_2 \end{array} \right] = \frac{\$L_3(L_1 + L_3) + R(L_1 + L_3)}{\$^2 R L_3 (L_1 + L_3)} - \frac{1}{\$^2 C^2}$$

$$\frac{\$L_3^2 (L_1 + L_3) + \$^2 L_3^2 R (L_1 + L_3) - \$^2 R L_3 (L_1 + L_3)}{\$^2 L_3^2 R (L_1 + L_3)}$$

$$\underline{Y}_{14} = \frac{\$L_3^2 (L_1 + L_3) + (L_1 + L_3)(R L_3 - R)}{\$^2 L_3^2 R (L_1 + L_3)} = \frac{\$L_3^2 + R(L_3 - 1)}{\$^2 L_3^2 R}$$

$$\frac{V_0}{V_i} = \frac{\frac{R}{L_1 L_3 C}}{\$^3 + \$^2 \frac{R}{L_3} + \frac{\$(L_1 + L_3)}{L_1 L_3 C} + \frac{R}{L_1 L_3 C}}$$